

# Electronics Laboratory

Winter semester 2025

---

## Lab 5 – Digital

Name \_\_\_\_\_ Reg. Nr. \_\_\_\_\_

Name \_\_\_\_\_ Reg. Nr. \_\_\_\_\_

Score and comments (only for tutors, please leave blank)

*Please fill out this cover sheet and submit it with your lab report.*



## 5 Lab 5 – Digital

### Introduction

In this one digital lab, we will use the components in the electronics kit for the analog labs and reconfigure them into a variety of digital circuits. In two measurement sections, we will first wire up a MOSFET-based inverter chain and then configure it as a ring oscillator. We will subsequently use the three MOSFETs in various configurations, with varying inputs and loads, to realize three different logic functions.

### Notes

- The simulations performed in this lab will use *LogiSim*, which is open source software available at [www.cburch.com/logisim/download.html](http://www.cburch.com/logisim/download.html). You should download, install and familiarize yourself with it before beginning with the digital modeling.
- Pay attention to the wiring conventions for NMOS and PMOS transistors in *LogiSim*, as shown in Figure 5.0.1. Note the direction of the caret ( $\wedge$ ) and do not confuse source and drain.

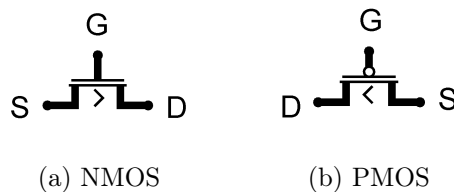


Figure 5.0.1: Wiring convention for FETs in *LogiSim*.



## 5.1 Preparation

Please answer the following questions *before* beginning with the simulations or experiments. Then complete the preparation quiz “Preparation 5.1 – Digital” on Ilias using your results. The points for this preparation section will only be awarded via Ilias.

### 5.1.1 Logic families

Review the different kind of loads (pull-ups) that can be used with an N-channel and P-channel MOSFETs to realize a simple inverter circuit.

### 5.1.2 Logic function

Write down a logic equation defining the logic function of the circuit shown in Figure 5.1.1 below.

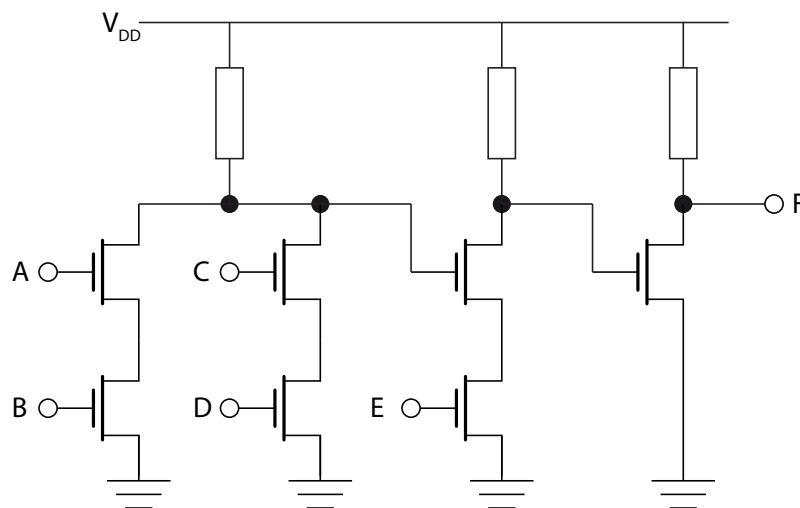


Figure 5.1.1

### 5.1.3 Ring oscillator

You are given a nine-stage ring oscillator, where each stage consists of an inverter with a switching delay time of  $55.55 \mu\text{s}$ . Calculate the oscillation frequency.

### 5.1.4 Longer ring oscillator

The oscillation frequency of the ring oscillator in Section 5.1.3 is too high, so you exactly double the number of stages. What is the oscillation frequency now?



### 5.1.5 Gate widths

Consider a 3-input CMOS NOR gate. If the pull-up MOSFETs have  $(\frac{W}{L})_{pu} = \frac{36}{2}$ , what is the optimal sizing for the pull-down MOSFETs,  $(\frac{W}{L})_{pd}$ ?



## 5.2 Ring oscillator

We will begin by simulating a three-inverter chain to see how basic logic simulation on transistor level works. We will then wire up and measure such an inverter chain and then make a ring oscillator from that. We will look at its oscillation speed and determine the propagation delay of each inverter.

### 5.2.1 Simulation

- (a) Using Logisim, set up a three-inverter ring oscillator.
- (b) Place a “pull resistor”<sup>1</sup>. Set its *Pull Direction* to *ONE* to create a pull-up resistor.
- (c) Place a ground below the pull up.
- (d) Place a MOSFET between the two (rotate to to face *North*). Set its *Type* to *N-TYPE*. Connect the drain to the pull resistor and the source to the ground.
- (e) Place a pin and attach it to the gate of the transistor. Set *Three-state?* to *NO*. Name this pin *Input* (under *label*).
- (f) Attach another pin to the drain of the transistor. Again set *Three-state?* to *NO* but set *Output?* to *YES*. Name this pin *Inv1*.
- (g) Using the “finger pointer” tool, toggle the input from 1 to 0 and back, and verify that the circuit acts as an inverter.
- (h) Copy everything (except the input pin) two more times and name the new output pins *Inv2* and *Inv3*.
- (i) Connect *Inv1* to the gate of the second transistor and *Inv2* to the gate of the third transistor, making a three-inverter chain.
- (j) Again verify that the circuit works as you expect.
- (k) Using *File/Export Image*, save two versions of this circuit<sup>2</sup>, one with input 1, the other with input 0; save these for your report.
- (l) Generate the truth table of this circuit (*Project/Analyze Circuit*). Make and crop a screen shot for your report.

---

<sup>1</sup>All the components you need for this part are found under “wiring”.

<sup>2</sup>Uncheck “Printer View” for a color image.



## 5.2.2 Measurement

For the measurements, we will use the three MOSFETs found in the “MOSFET” section of the electronics board, one in the *MOSFET characteristics* circuit, shown in Figure 5.2.1, and two in the *MOSFET logic gates* circuit, shown in Figure 5.2.2.

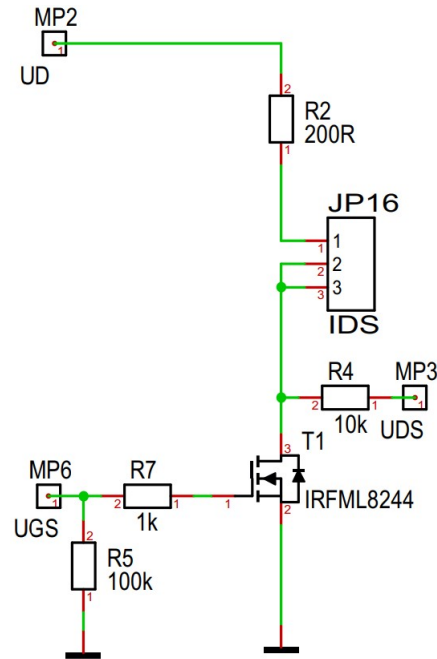


Figure 5.2.1: Schematic of the *MOSFET characteristics* circuit

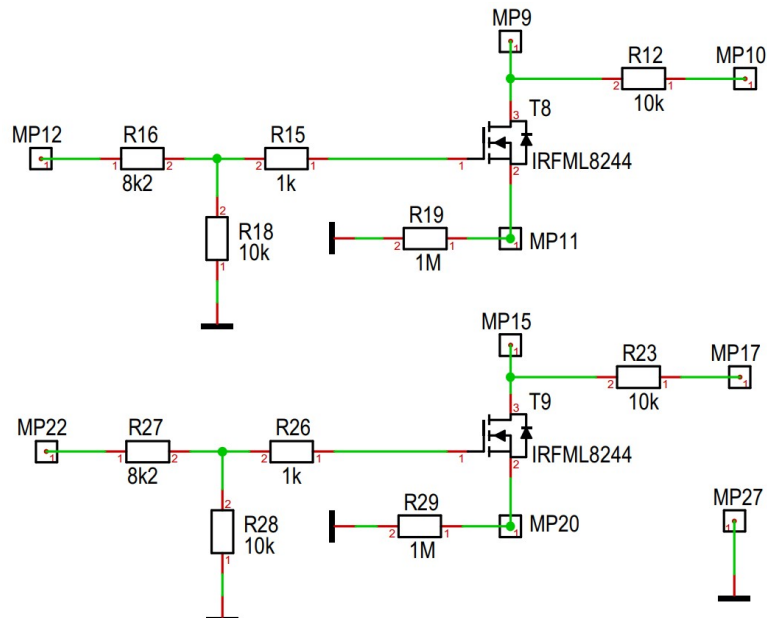


Figure 5.2.2: Schematic of the *MOSFET logic gates* circuit

In the first part of this measurement section, we will first connect three inverters (with active pull-down and passive pull-up) in series:  $T1$  is the first inverter;  $T8$  the second; and  $T9$  the third. We will record the logic functions of the individual signals and determine the propagation delay. In the second part, we will then realize a ring oscillator by connecting the output of inverter 3 back to the input of inverter 1.

### Inverter chain

- (a) Connect  $MP3$ ,  $MP10$  and  $MP17$  to the output of the AC power amplifier ( $MP35$ ) to supply the passive pull-up of all three inverters.
- (b) Connect  $MP11$  and  $MP20$  to  $GND$  ( $MP27$ ) for the active pull-down of the second and third inverters; the source of  $T1$  is already at  $GND$ .
- (c) Connect the output of the first inverter ( $PIN2$  of jumper  $JP16$ ) to the input of the second inverter ( $MP12$ ).
- (d) Connect the output of the second inverter ( $MP9$ ) to the input of the third inverter ( $MP22$ ).
- (e) On the USB-XLAB there are two pin rows with the digital input and output pins  $DI\_0/DO\_0$  to  $DI\_15/DO\_15$ , where the inputs are on the left pin row (blue) and the outputs are on the right pin row (black). Connect the inputs  $DI\_0$  to  $MP69$ ,  $DI\_1$  to  $MP12$ ,  $DI\_2$  to  $MP22$  and  $DI\_3$  to  $MP15$ . This way, the input signal as well as the individual output signals are sampled.
- (f) Create corresponding digital channels in *WaveForms/Scope*. To do this, select *Add Channel/Digital/Signal* on the right-hand side and successively name  $DIO\ 0\ Vin$ ,  $DIO\ 1\ Inv1$ ,  $DIO\ 2\ Inv2$  and  $DIO\ 3\ Inv3$ .
- (g) Set the time scale to  $5\ \mu s/div$ .
- (h) Connect the control signal of  $W1$  ( $MP69$ ) to the input of the first inverter at  $MP6$ .
- (i) Apply the  $5\ V$  of  $MP32$  to the  $Ux2$  input of the AC power amplifier ( $MP40$ ) to switch on the voltage supply of the pull-ups.
- (j) Set up a PWM signal in *WaveForms/Wavegen* with  $25\ kHz$ , a duty cycle of  $50\ \%$  and a voltage of  $0\ V$  to  $5\ V$ .
- (k) Create the truth table for the input signal  $V_{in}$  and the three outputs  $Inv_1$ ,  $Inv_2$  and  $Inv_3$ .
- (l) Measure (by double left-clicking on the digital area) the delay  $t_{pd,rise}$  ( $t_{pd,fall}$ ) from  $V_{in}$  to  $Inv_3$  with a rising (falling) edge of  $V_{in}$ . Sum up both values and determine a frequency from this time. This is an estimate of the frequency of the ring oscillator which we will see in the next measurement task.



## Ring oscillator

- (m) Start with the circuit from the previous task.
- (n) Remove the connection between *MP32* and *MP40* to switch off the power supply to the pull-ups while the circuit is being converted.
- (o) Switch off the signal of the wavegen *W1* and then remove the connection between *W1* (*MP69*) and the input of the first inverter (*MP6*).
- (p) Connect the output of the third inverter (*MP15*) to the input of the first inverter (*MP6*) to close the ring oscillator.
- (q) Apply the 5 V of *MP32* to the *Ux2* input of the AC power amplifier (*MP40*) to switch on the voltage supply of the pull-ups.
- (r) Measure for each inverter  $i \in [1, 2, 3]$ : The duration for which the signal of a cycle is low ( $t_{L,i}$ ) or high ( $t_{H,i}$ ) and calculate the period  $\tau_i$  and frequency  $f_i$  as well as the duty cycle  $p_i$  (for signal high).
- (s) Compare the frequencies  $f_i$  with each other as well as with the estimated value of the previous task.
- (t) Determine which duty cycle of the three signals is closest to 50 %. Connect its signal/pin to the first input of the oscilloscope (*MP72*).
- (u) Measure and plot the analogue and the digital signal course over a period of  $2.2 \cdot \tau_i$  in a diagram, each with its own ordinate (y-axis). Explicitly address their shape and compare both signals.





## 5.3 NMOS logic

We will simulate and then construct and measure three different NMOS logic gates using three MOSFETs in varying configurations.

### 5.3.1 Simulation

#### Logic circuit 1

- (a) Place three N-type MOSFETs with one input pin each ( $A$ ,  $B$  and  $C$ ) at their gates.
- (b) Connect all sources to ground.
- (c) Connect all the drains together, with a single pull-up resistor and a single output pin labeled  $D$ .
- (d) Save a copy of the schematic of this circuit (*File/Export Image*) for your report.
- (e) Generate the truth table of this circuit (*Project/Analyze Circuit*). Make and crop a screen shot for your report.
- (f) Is this a standard logic gate and, if so, which one?

#### Logic circuit 2

- (g) Again place three N-type MOSFETs with one input pin each ( $A$ ,  $B$  and  $C$ ) at their gates.
- (h) Connect the source of the first transistor to the drain of the second and the source of the second to the drain of the third transistor.
- (i) Connect the source of the third transistor to ground.
- (j) Connect the drain of the first transistor to a single pull-up resistor and a single output pin called  $D$ .
- (k) Save a copy of the schematic of this circuit (*File/Export Image*) for your report.
- (l) Generate the truth table of this circuit (*Project/Analyze Circuit*). Make and crop a screen shot for your report.
- (m) Is this a standard logic gate and, if so, which one?

#### Logic circuit 3

- (n) Finally, again place three N-type MOSFETs with one input pin each ( $A$ ,  $B$  and  $C$ ) at their gates.
- (o) Connect the source of the first transistor to the drain of the second transistor.



- (p) Connect the source of the second and third transistors to ground.
- (q) Connect the drain of the first and third transistors with each other, with a single pull-up resistor and a single output pin called *D*.
- (r) Save a copy of the schematic of this circuit (*File/Export Image*) for your report.
- (s) Generate the truth table of this circuit (*Project/Analyze Circuit*). Make and crop a screen shot for your report.
- (t) Is this a standard logic gate and, if not, what is the logic formula of this circuit?

### 5.3.2 Measurement

We will again use the three MOSFETs found in the “MOSFET” section of the electronics board, one in the *MOSFET characteristics* circuit, shown in Figure 5.2.1, and two in the *MOSFET logic gates* circuit, shown in Figure 5.2.2.

#### Logic circuit 1

- (a) Connect *MP17* to the output of the AC amplifier (*MP35*) for the supply of the passive pull-up. Then connect *MP11* and *MP20* to *GND* (e.g. *MP27*) for the active pull-down of both MOSFETs.
- (b) Connect the digital outputs of the USB-XLAB to the inputs of the MOSFETs: *DO\_0* with *MP6*, *DO\_1* with *MP12* and *DO\_2* with *MP22*. Then connect the digital input of the USB-XLAB to the output of the MOSFET *T9*: *DI\_8* with *MP15*.
- (c) Short-circuit *MP9*, *MP15* and *PIN2* of jumper *JP16* with each other.
- (d) Apply the 5 V of *MP32* to the *Ux2* input of the AC amplifier (*MP40*) to switch on the voltage supply of the pull-ups.
- (e) In *WaveForms*, open the menu *Static IO*, in which the digital input and output pins can be statically controlled or read.
  - Click *DIO 15-8* on the left and then select *Bit IO/LED* to set pins 8 to 15 as inputs to represent their values as LEDs.
  - Click *DIO 7-0* on the left and then select *Bit IO/Switch/Push/Pull (1/0)* to set pins 0 to 7 as output to adjust their values using sliders.
- (f) Select *Control/Run* to start the application.
- (g) Determine the truth table of this circuit by setting *DIO 0*, *DIO 1* and *DIO 2* and reading *DIO 8*.



## Logic circuit 2

- (h) Connect *MP17* to the output of the AC amplifier (*MP35*) for the supply of the passive pull-up. Then connect the digital outputs of the USB-XLAB to the inputs of the MOSFETs: *DO\_0* with *MP6*, *DO\_1* with *MP12* and *DO\_2* with *MP22*.
- (i) Connect the digital input of the USB-XLAB to the output of the MOSFET *T9*: *DI\_8* with *MP15*.
- (j) Short circuit *MP20* and *MP9* with each other and short circuit *MP11* and *PIN2* of Jumper *JP16* with each other.
- (k) Apply the 5 V of *MP32* to the *Ux2* input of the AC amplifier (*MP40*) to switch on the voltage supply of the pull-ups.
- (l) In *WaveForms*, open the menu *Static IO*, in which the digital input and output pins can be statically controlled or read.
  - Click *DIO 15-8* on the left and then select *Bit IO/LED* to set pins 8 to 15 as inputs to represent their values as LEDs.
  - Click *DIO 7-0* on the left and then select *Bit IO/Switch/Push/Pull (1/0)* to set pins 0 to 7 as output to adjust their values using sliders.
- (m) Select *Control/Run* to start the application.
- (n) Determine the truth table of this circuit by setting *DIO 0*, *DIO 1* and *DIO 2* and reading *DIO 8*.

## Logic circuit 3

- (o) Connect *MP17* to the output of the AC amplifier (*MP35*) for the supply of the passive pull-up. Then connect *MP11* to *GND* (e.g. *MP27*) for the active pull-down.
- (p) Connect the digital outputs of the USB-XLAB to the inputs of the MOSFETs: *DO\_0* with *MP6*, *DO\_1* with *MP12* and *DO\_2* with *MP22*. Then connect the digital input of the USB-XLAB to the output of the MOSFET *T9*: *DI\_8* with *MP15*.
- (q) Short circuit *MP20* and *MP9* with each other and short circuit *MP15* and *PIN2* of Jumper *JP16* with each other.
- (r) Apply the 5 V of *MP32* to the *Ux2* input of the AC amplifier (*MP40*) to switch on the voltage supply of the pull-ups.
- (s) In *WaveForms*, open the menu *Static IO*, in which the digital input and output pins can be statically controlled or read.
  - Click *DIO 15-8* on the left and then select *Bit IO/LED* to set pins 8 to 15 as inputs to represent their values as LEDs.



- Click *DIO 7-0* on the left and then select *Bit IO/Switch/Push/Pull (1/0)* to set pins 0 to 7 as output to adjust their values using sliders.
- (t) Select *Control/Run* to start the application.
- (u) Determine the truth table of this circuit by setting *DIO 0*, *DIO 1* and *DIO 2* and reading *DIO 8*.

